

Chapter 3

Sequential Logic Design

 


Figure 3.1 Cross-coupled inverter pair

 


Figure 3.2 Bistable operation of cross-coupled inverters

 


Figure 3.3 SR latch schematic

 
 


Figure 3.4 Bistable states of SR latch

Case	S	R	Q	\overline{Q}
IV	0	0	Q_{prev}	\overline{Q}_{prev}
I	0	1	0	1
II	1	0	1	0
III	1	1	0	0

Figure 3.5 SR latch truth table


 



Figure 3.6 SR latch symbol

 

(a)

CLK	D	\overline{D}	S	R	Q	\overline{Q}
0	X	\overline{X}	0	0	Q_{prev}	\overline{Q}_{prev}
1	0	1	0	1	0	1
1	1	0	1	0	1	0

(b)

 

(c)

Figure 3.7 D latch: (a) schematic, (b) truth table, (c) symbol

 
 
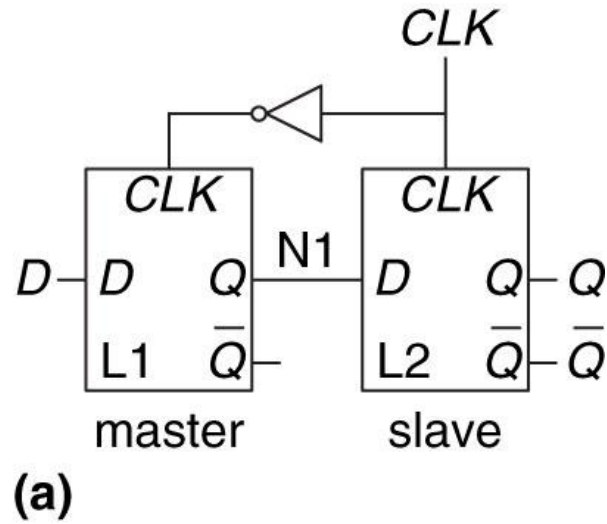


Figure 3.8 D flip-flop: (a) schematic, (b) symbol, (c) condensed symbol

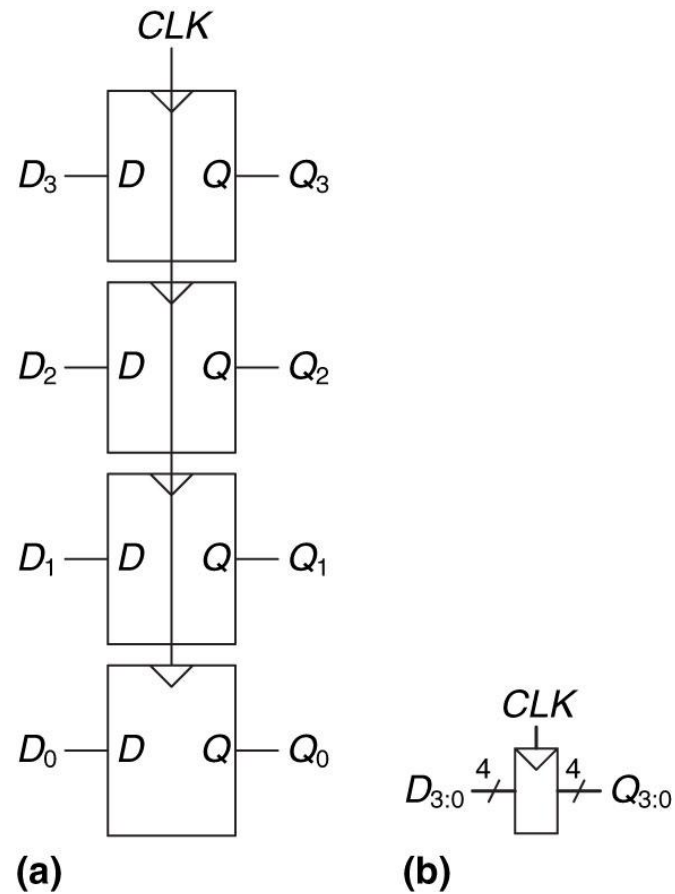


Figure 3.9 A 4-bit register: (a) schematic and (b) symbol



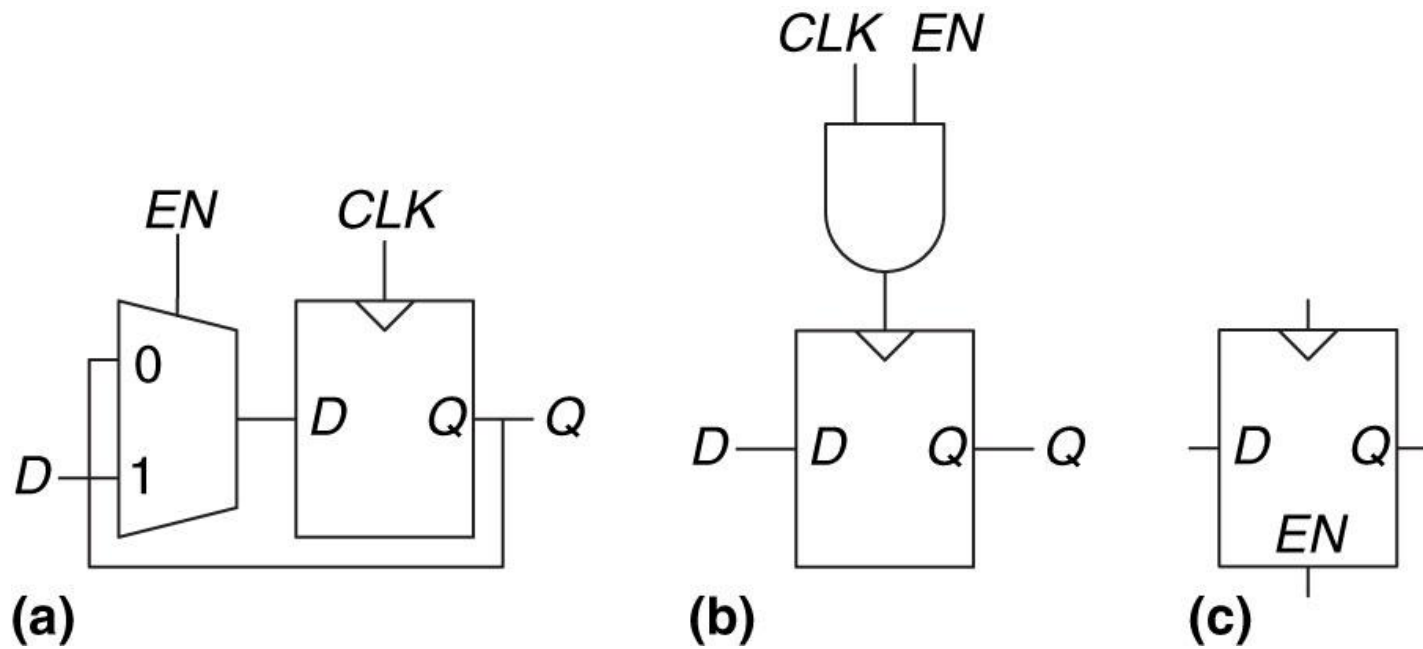



Figure 3.10 Enabled flip-flop: (a, b) schematics, (c) symbol

 

(a)

 


(b)

 


(c)

Figure 3.11 Synchronously resettable flip-flop: (a) schematic, (b, c) symbols

 

(a)

 

(b)

Figure 3.12 D latch schematic

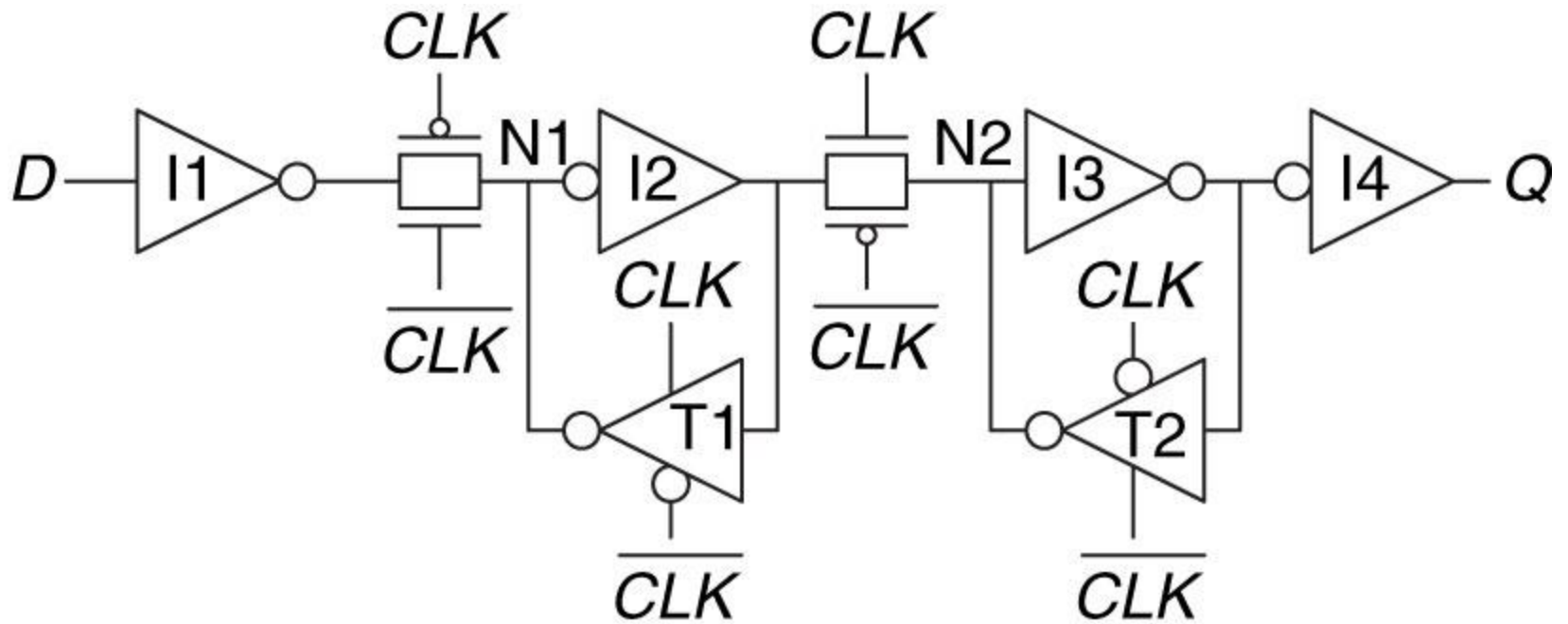


Figure 3.13 D flip-flop schematic

 


Figure 3.14 Example waveforms

 


Figure 3.15 Solution waveforms

 


Figure 3.16 Three-inverter loop

 


Figure 3.17 Ring oscillator waveforms

CLK	D	Q_{prev}	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$Q = CLK \cdot D + \overline{CLK} \cdot Q_{prev}$$

 


Figure 3.18 An improved (?) D latch

 


Figure 3.19 Latch waveforms illustrating race condition

 


Figure 3.20 Flip-flop current state and next state



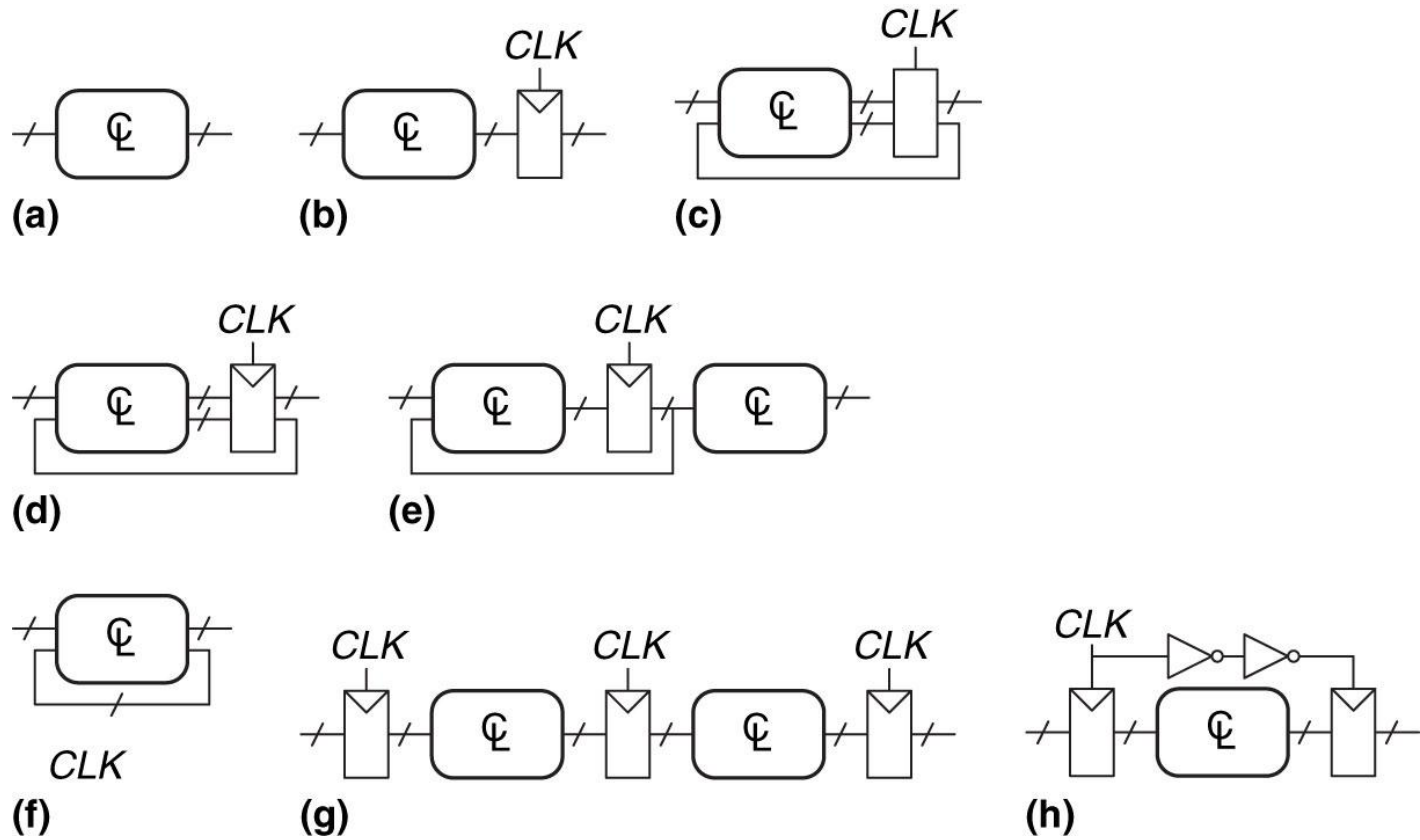


Figure 3.21 Example circuits

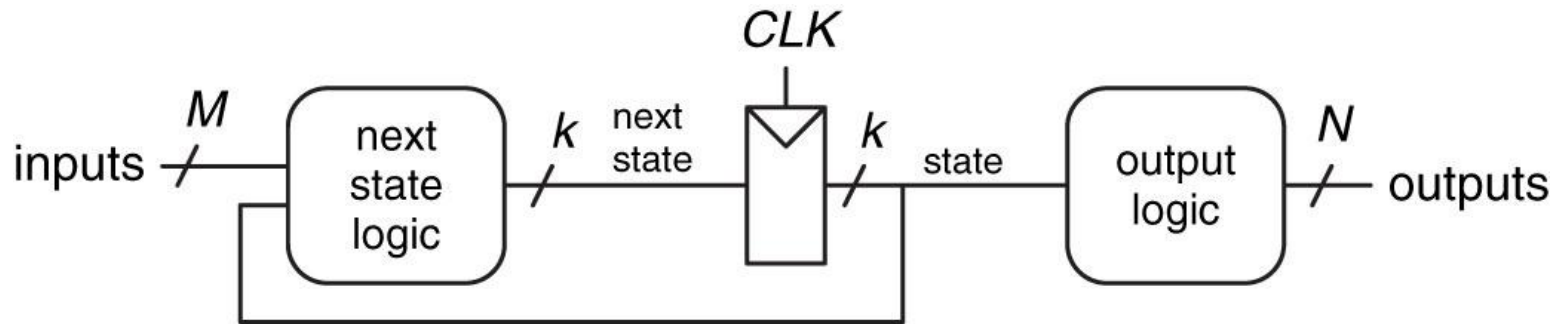

(a)

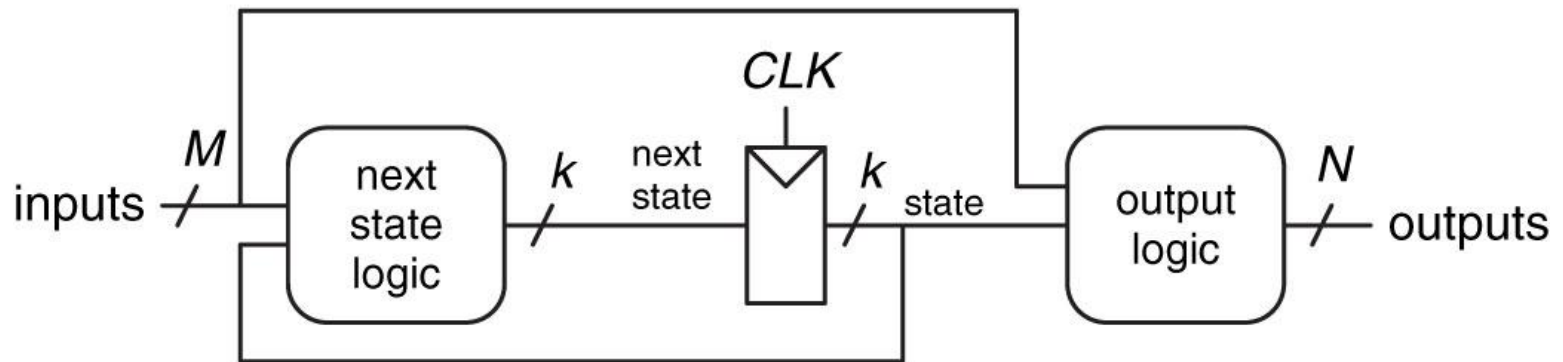

(b)

Figure 3.22 Finite state machines: (a) Moore machine, (b) Mealy machine

 


Figure 3.23 Campus map

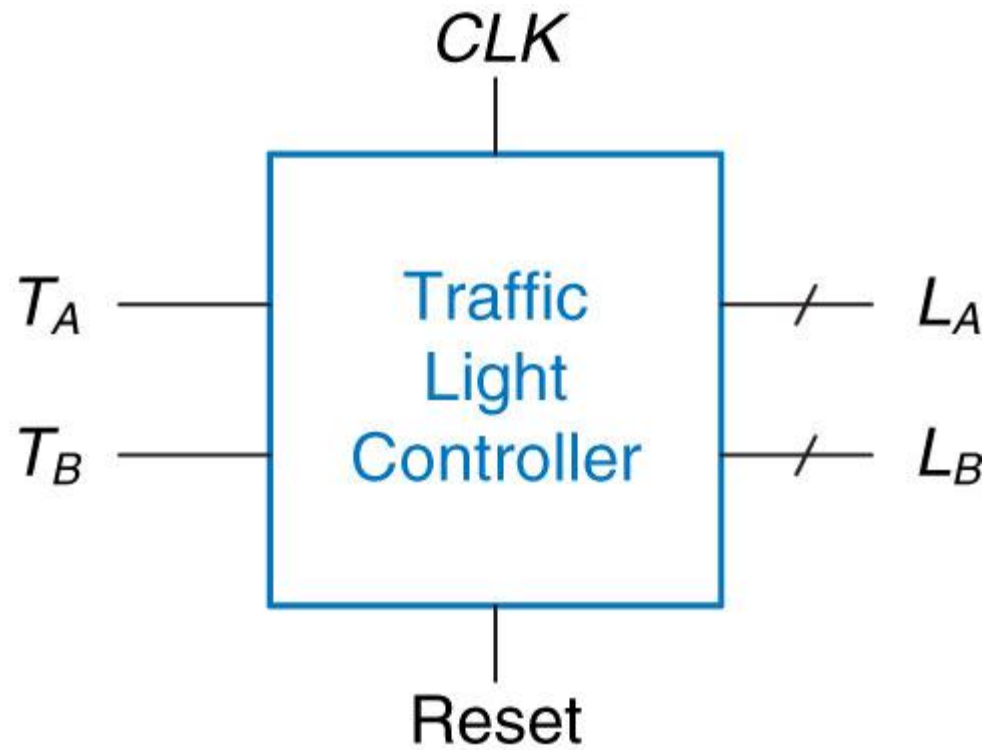


Figure 3.24 Black box view of finite state machine

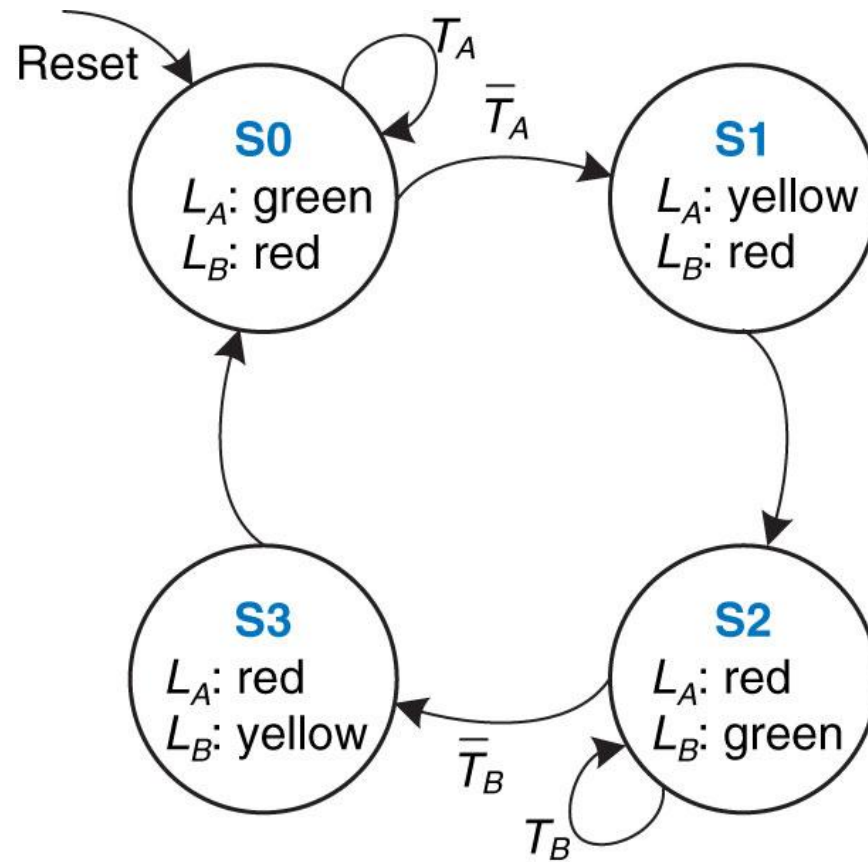


Figure 3.25 State transition diagram

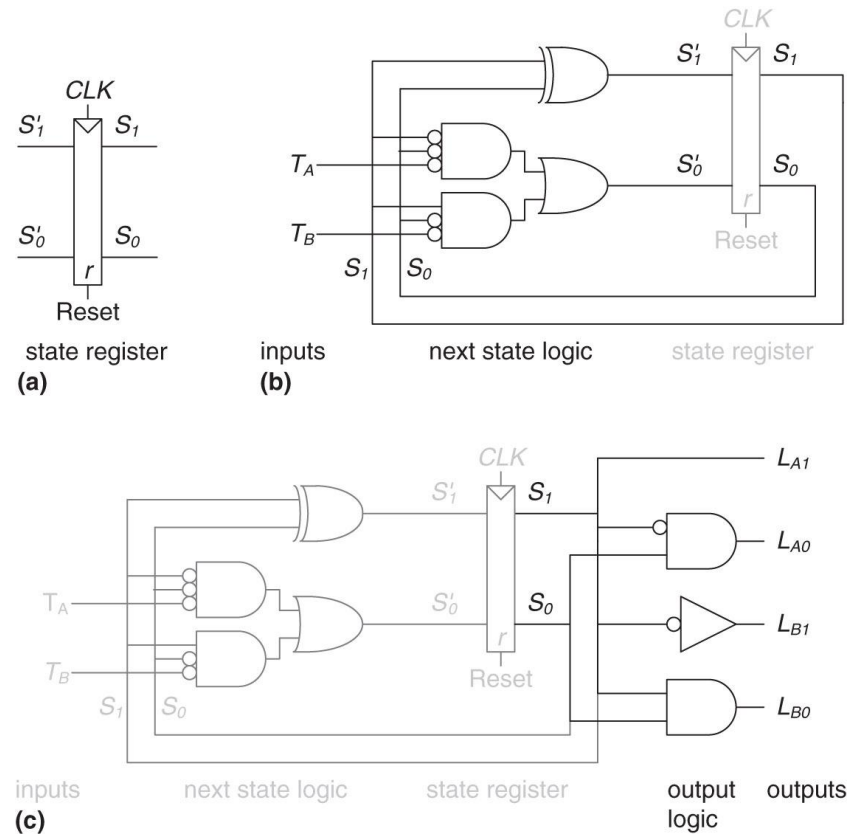


Figure 3.26 State machine circuit for traffic light controller

 


Figure 3.27 Timing diagram for traffic light controller



 


Figure 3.28 Divide-by-3 counter (a) waveform and (b) state transition diagram

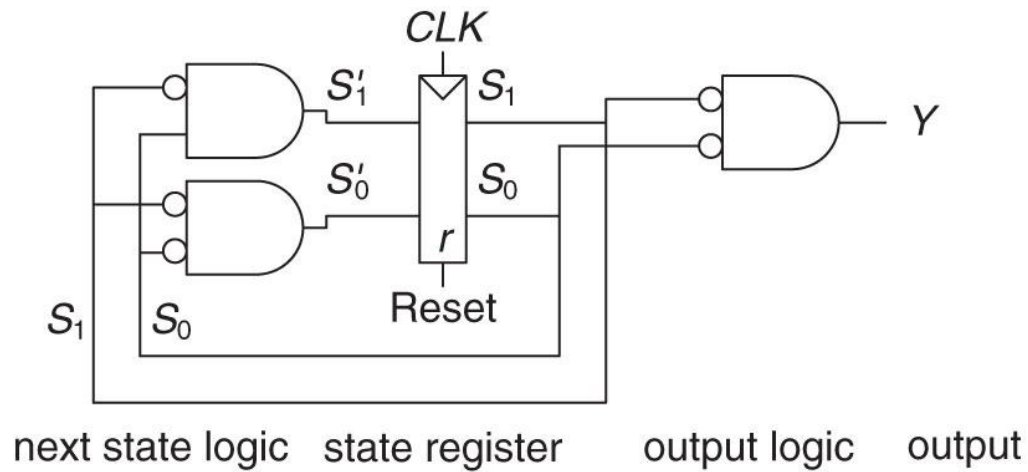

(a)

 

(b)

Figure 3.29 Divide-by-3 circuits for (a) binary and (b) one-hot encodings



 
 


Figure 3.30 FSM state transition diagrams: (a) Moore machine, (b) Mealy machine

 

(a)

 

(b)

Figure 3.31 FSM schematics for (a) Moore and (b) Mealy machines

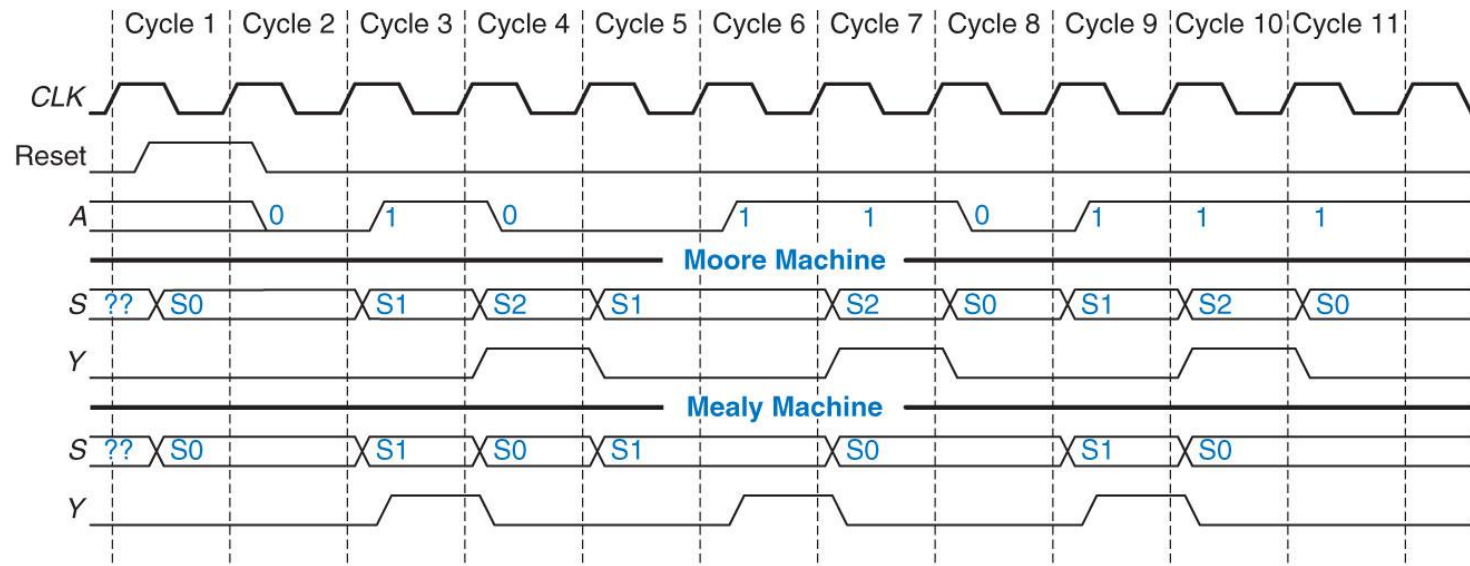


Figure 3.32 Timing diagrams for Moore and Mealy machines



 


Figure 3.33 (a) single and (b) factored designs for modified traffic light controller FSM

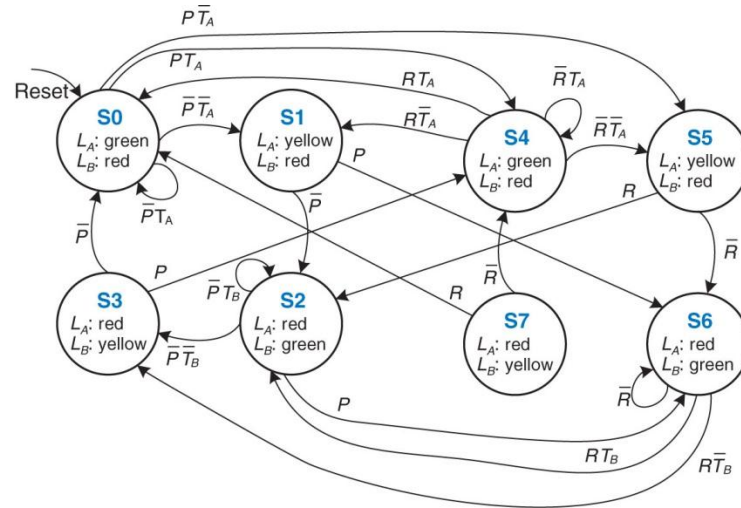

(a)

 

(b)

Figure 3.34 State transition diagrams: (a) unfactored, (b) factored

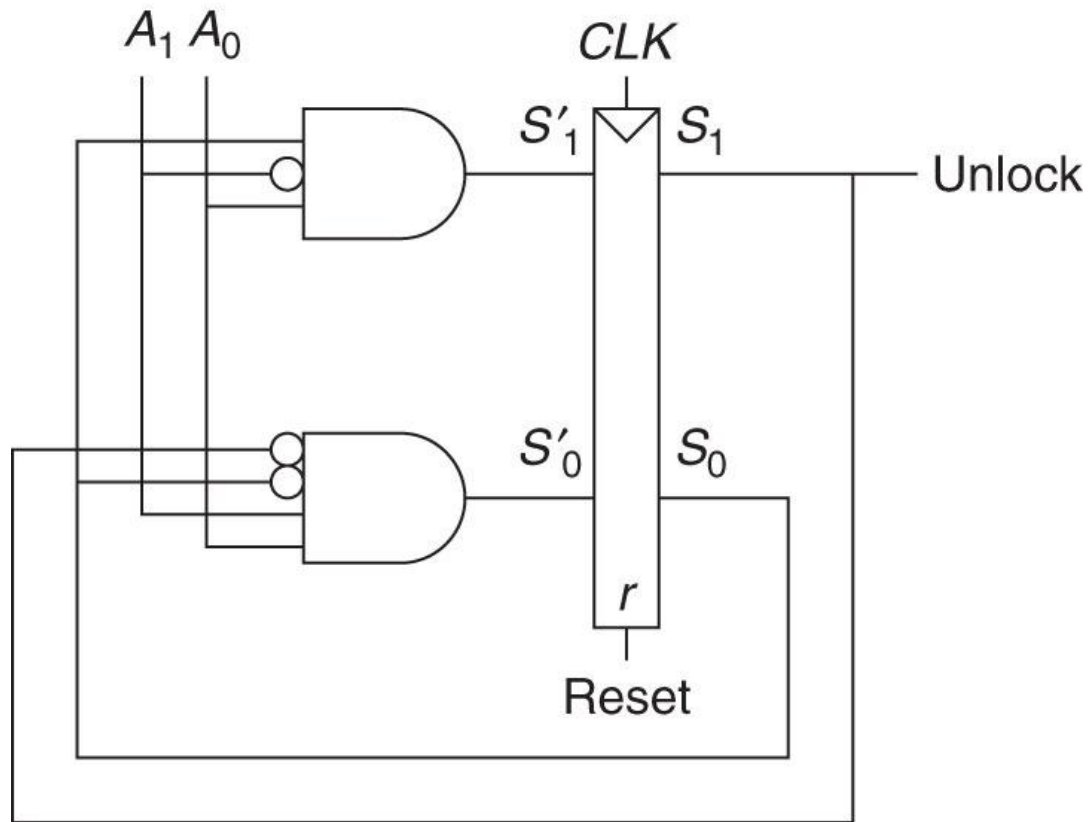


Figure 3.35 Circuit of found FSM for Example 3.9

 


Figure 3.36 State transition diagram of found FSM from Example 3.9

 


Figure 3.37 Timing specification for synchronous sequential circuit

 
 


Figure 3.38 Path between registers and timing diagram

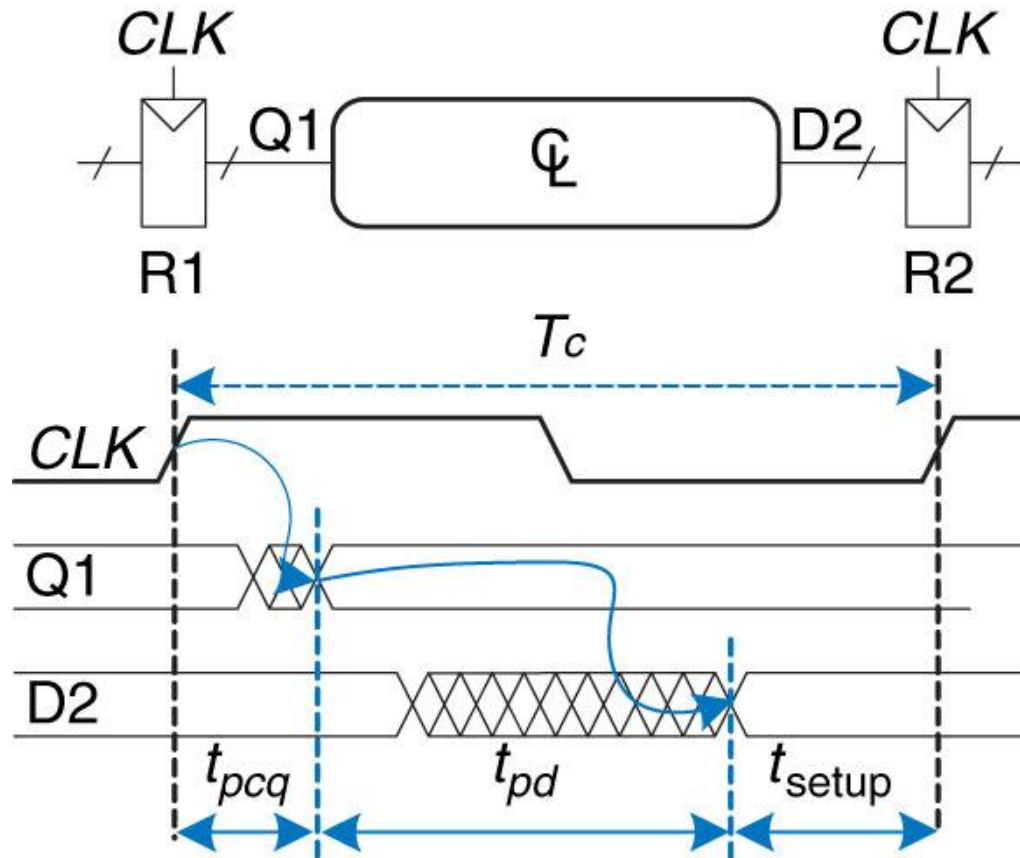


Figure 3.39 Maximum delay for setup time constraint

 


Figure 3.40 Minimum delay for hold time constraint

 


Figure 3.41 Back-to-back flip-flops

 


Figure 3.42 Sample circuit for timing analysis

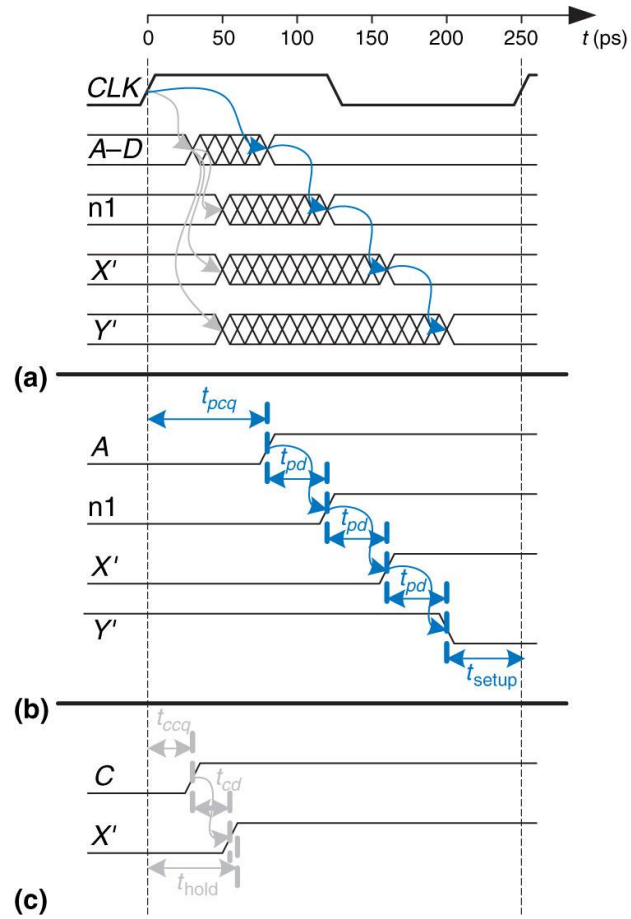


Figure 3.43 Timing diagram: (a) general case, (b) critical path, (c) short path

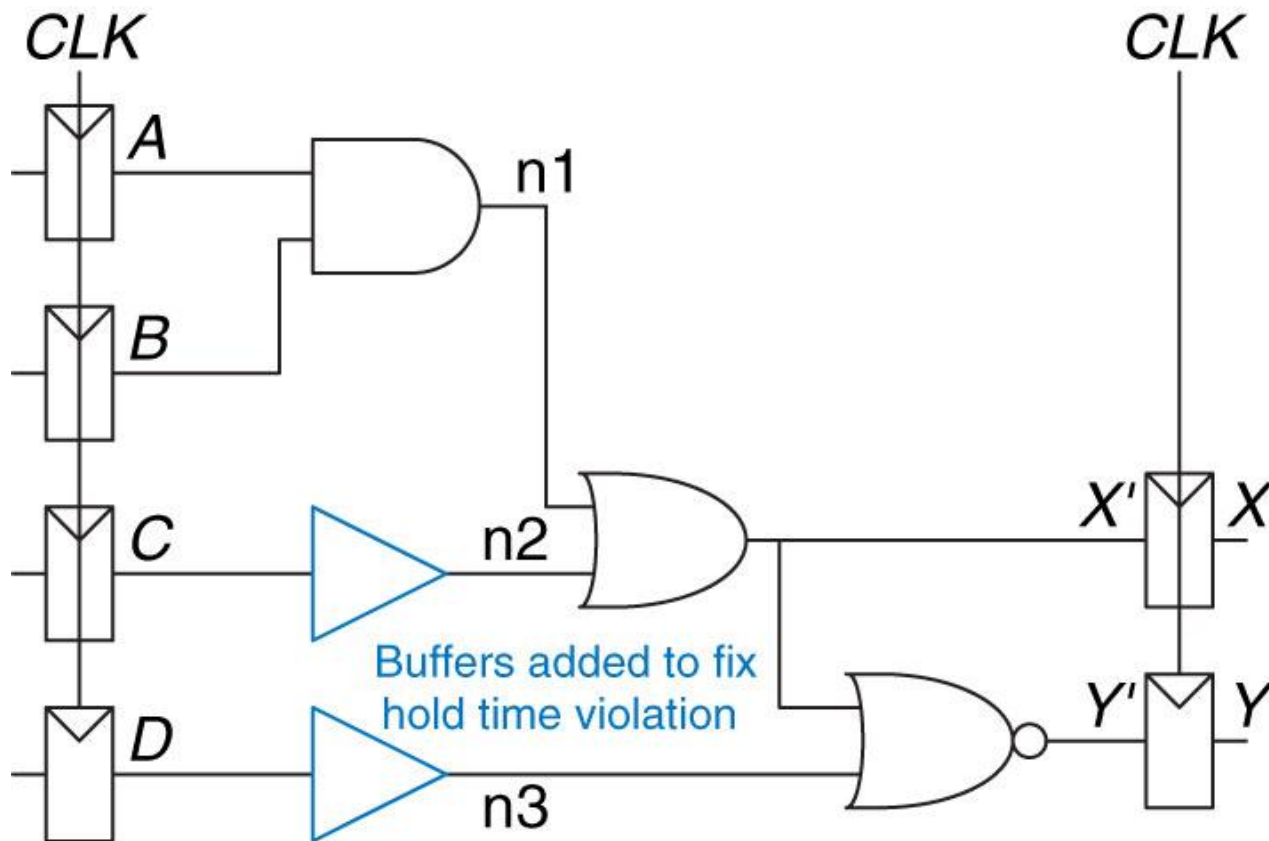


Figure 3.44 Corrected circuit to fix hold time problem

 


Figure 3.45 Timing diagram with buffers to fix hold time problem

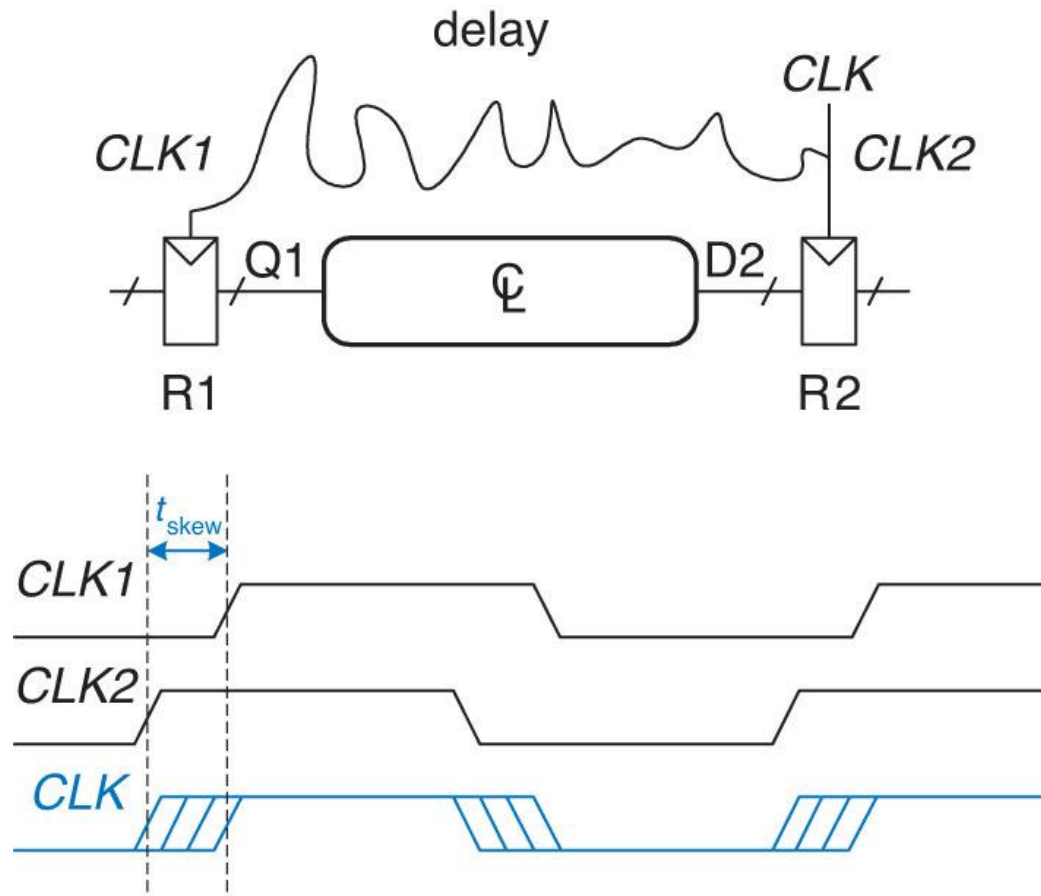


Figure 3.46 Clock skew caused by wire delay

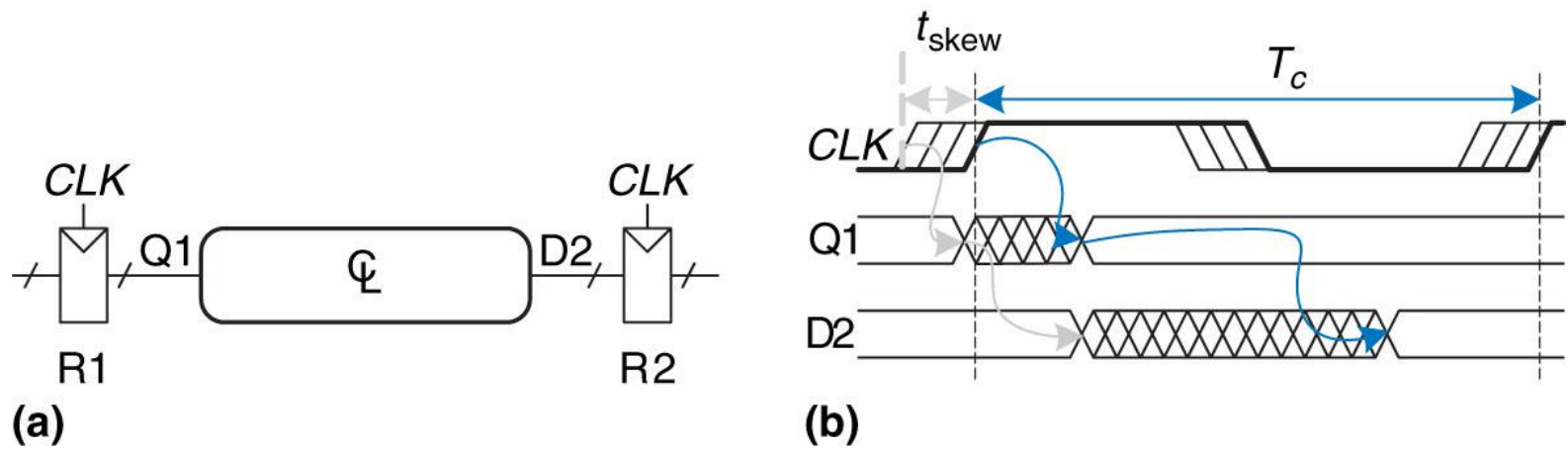


Figure 3.47 Timing diagram with clock skew

 


Figure 3.48 Setup time constraint with clock skew

 


Figure 3.49 Hold time constraint with clock skew

 


Figure 3.50 Input changing before, after, or during aperture

 


Figure 3.51 Stable and metastable states

 


Figure 3.52 Synchronizer symbol

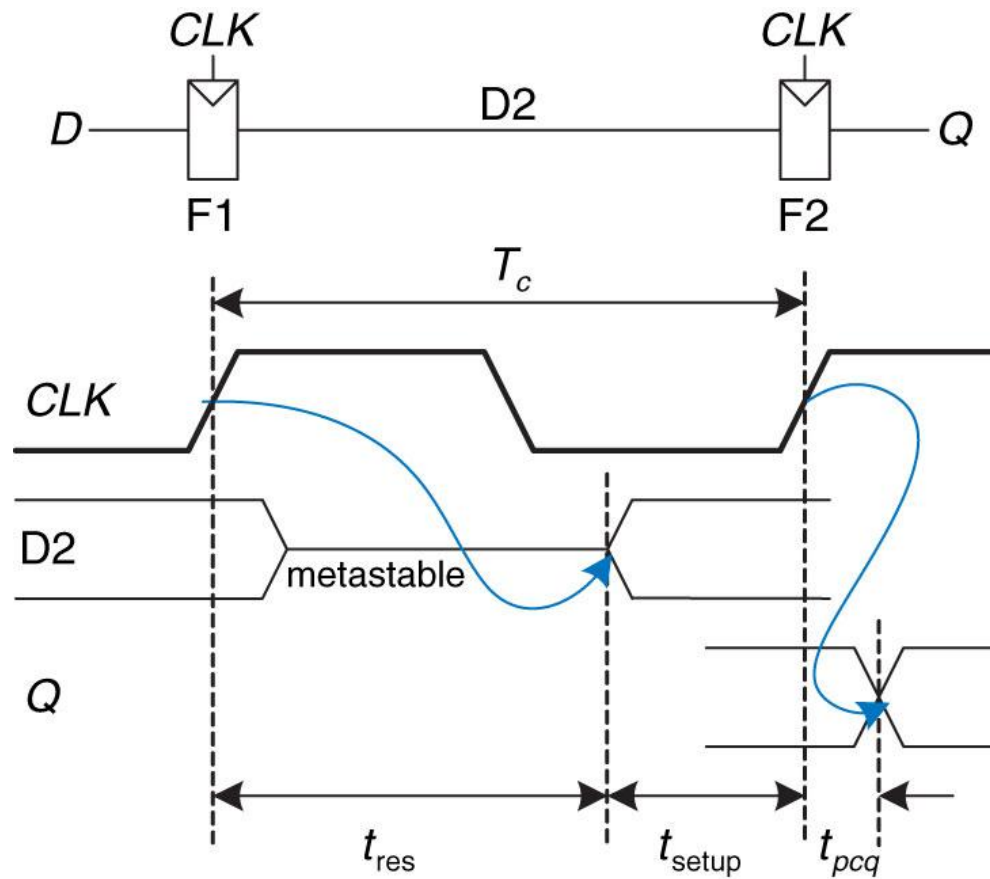


Figure 3.53 Simple synchronizer

 


Figure 3.54 Input timing

 


Figure 3.55 Circuit model of bistable device

 


Figure 3.56 Resolution trajectories

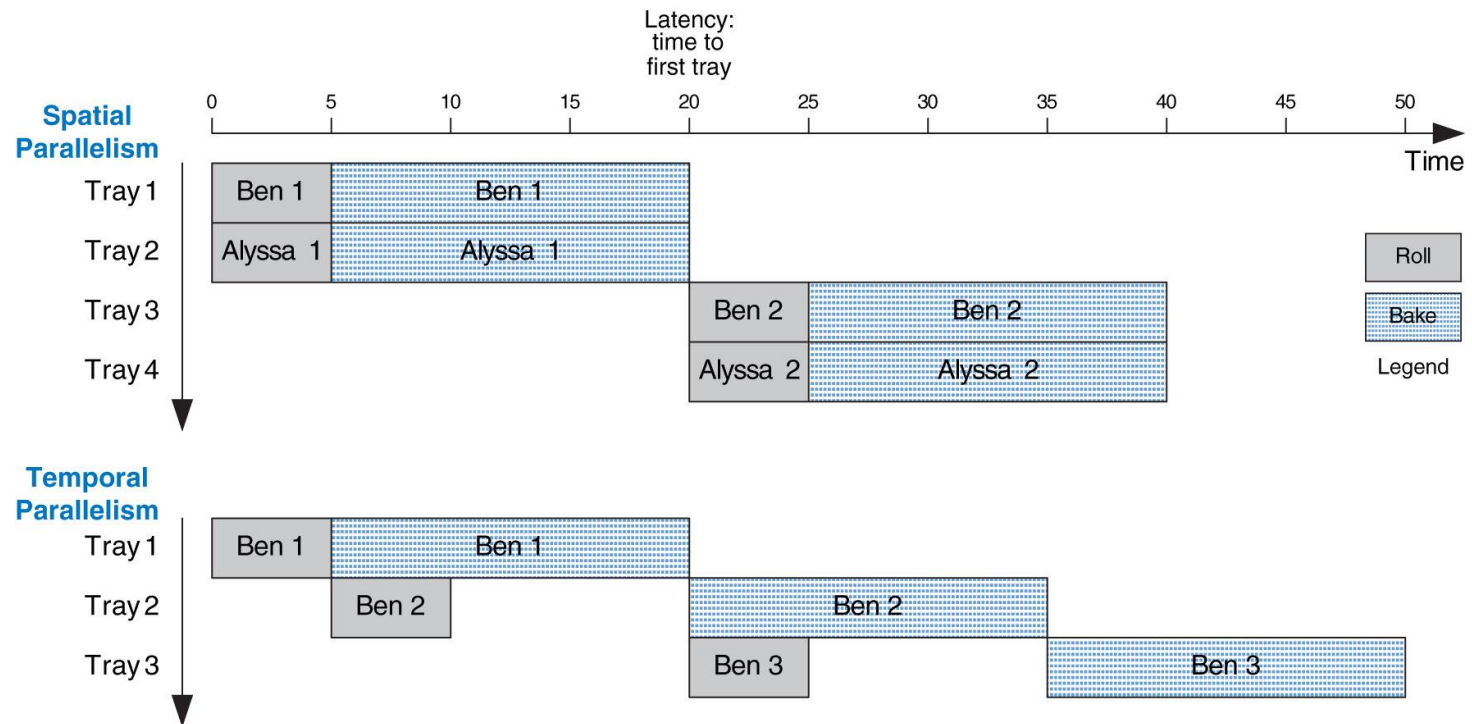


Figure 3.57 Spatial and temporal parallelism in the cookie kitchen

 


Figure 3.58 Circuit with no pipelining

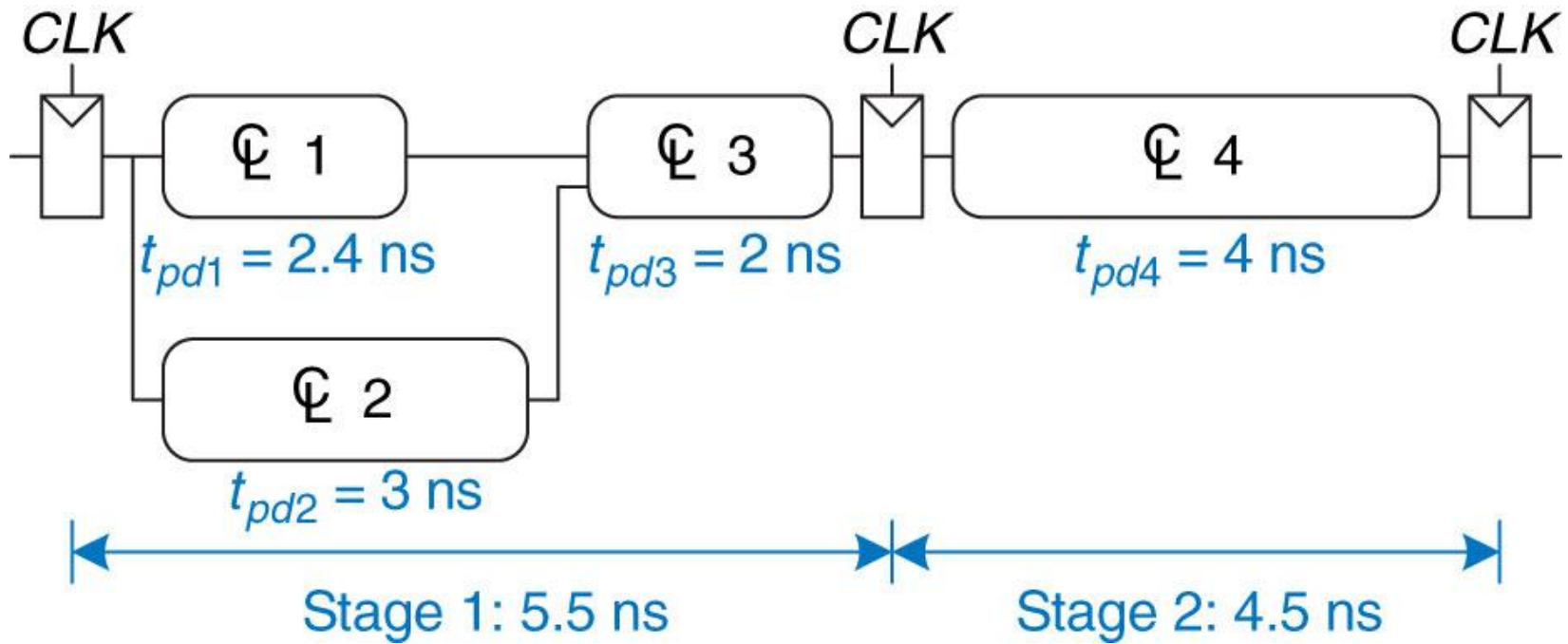


Figure 3.59 Circuit with two-stage pipeline

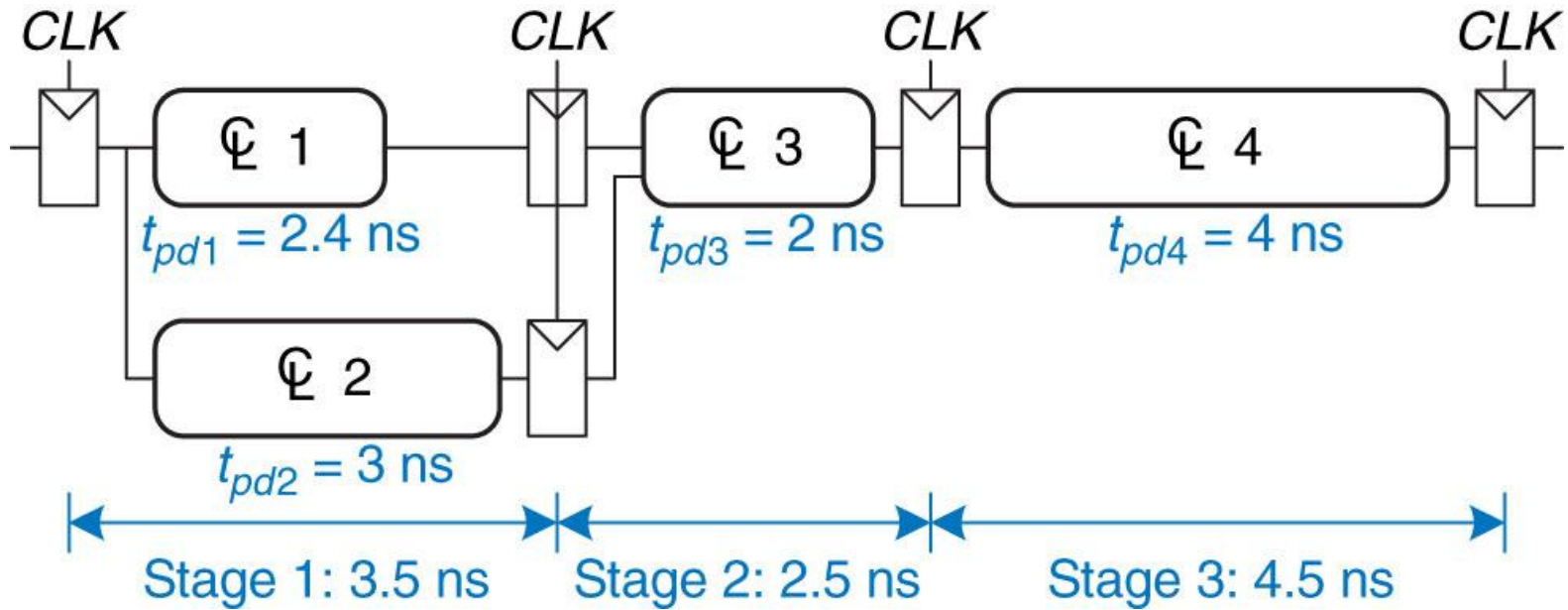


Figure 3.60 Circuit with three-stage pipeline

 


Figure 3.61 Input waveforms of SR latch for Exercise 3.1

 


Figure 3.62 Input waveforms of SR latch for Exercise 3.2

 


Figure 3.63 Input waveforms of D latch or flip-flop for Exercises 3.3 and 3.5

 


Figure 3.64 Input waveforms of D latch or flip-flop for Exercises 3.4 and 3.6

 


Figure 3.65 Mystery circuit

 


Figure 3.66 Mystery circuit

 


Figure 3.67 Muller C-element

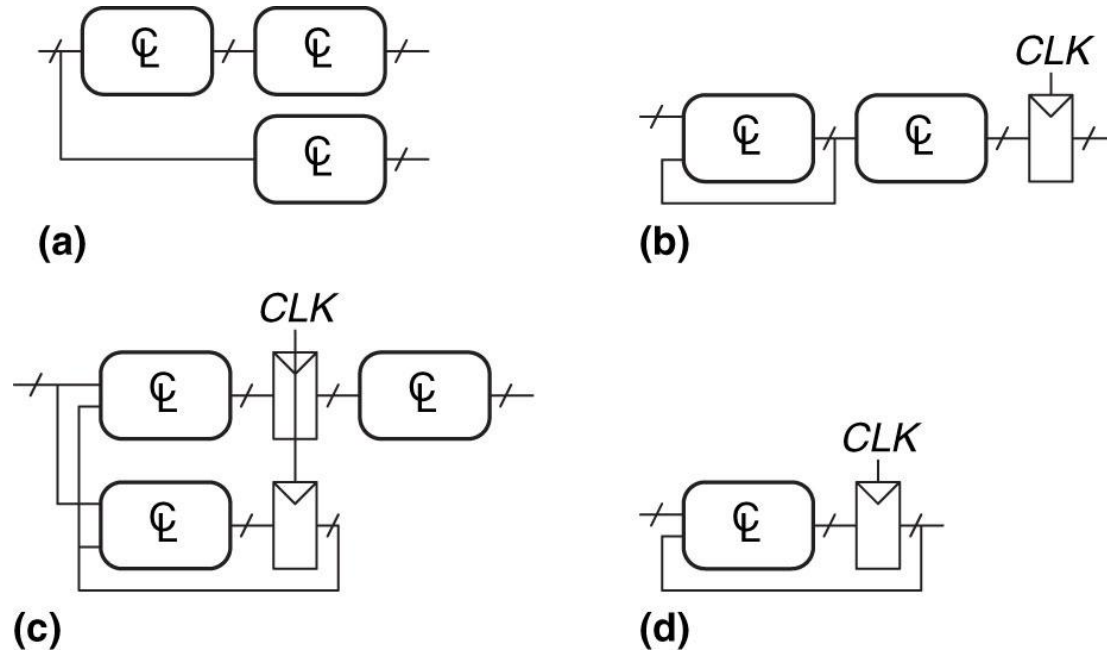


Figure 3.68 Circuits

 


Figure 3.69 State transition diagram

 


Figure 3.70 State transition diagram

 


Figure 3.71 FSM input waveforms

 


Figure 3.72 FSM schematic

 


Figure 3.73 FSM schematic

 


Figure 3.74 Registered four-input XOR circuit

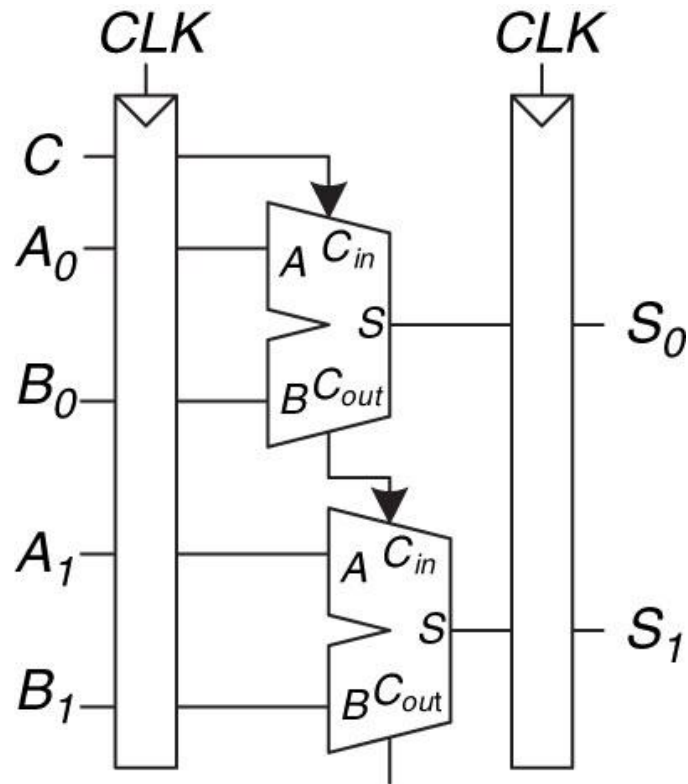


Figure 3.75 2-bit adder schematic

 


Figure 3.76 · New and improved · synchronizer

 


Figure 3.77 Signal waveforms

 


Figure M 01

 


Figure M 02




Figure M 03



Figure M 04



Figure M 05

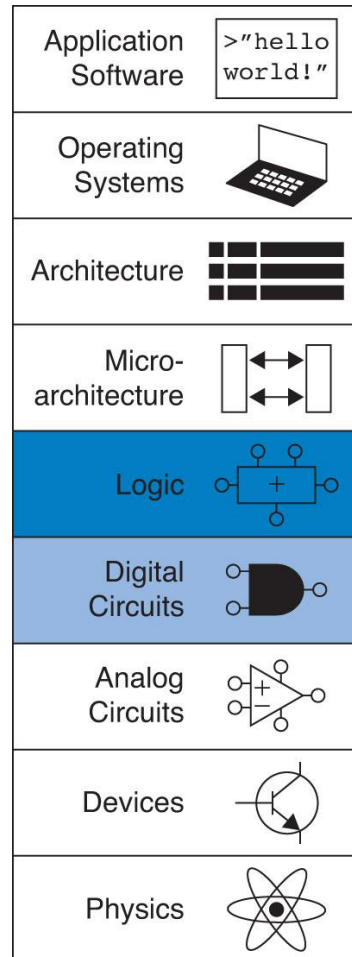

UNN Figure 1