

Chapter 2

Combinational Logic Design

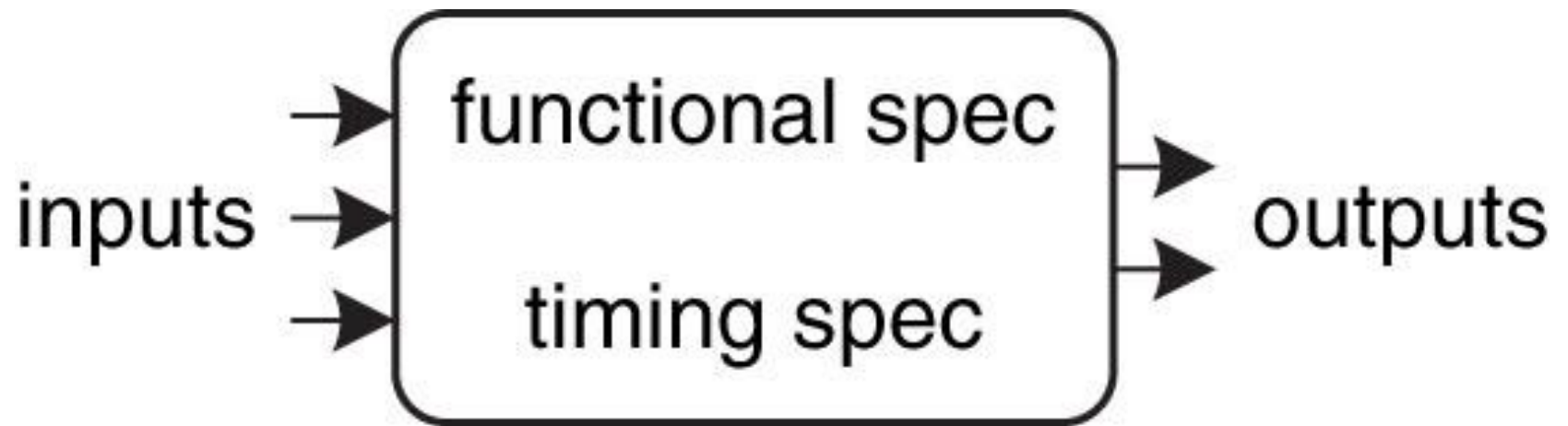


Figure 2.1 Circuit as a black box with inputs, outputs, and specifications



 


Figure 2.2 Elements and nodes

 


$$Y = F(A, B) = A + B$$

Figure 2.3 Combinational logic circuit

 


(a)

 

(b)

Figure 2.4 Two OR implementations

 

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Figure 2.5 Multiple-output combinational circuit

 
 


Figure 2.6 Slash notation for multiple signals

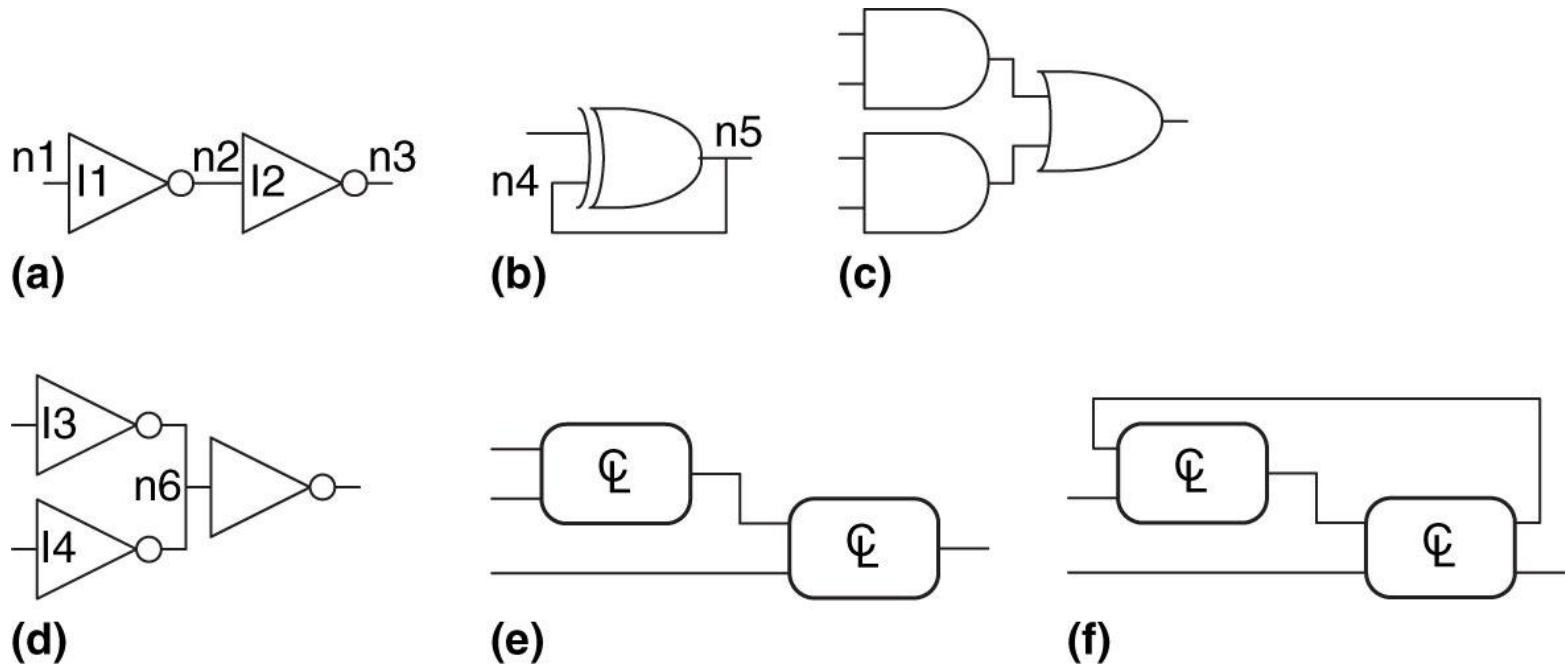


Figure 2.7 Example circuits

A	B	Y	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	0	$A B$	m_3


Figure 2.8 Truth table and minterms

A	B	Y	minterm	minterm name
0	0	0	$\bar{A} \bar{B}$	m_0
0	1	1	$\bar{A} B$	m_1
1	0	0	$A \bar{B}$	m_2
1	1	1	$A B$	m_3


Figure 2.9 Truth table with multiple TRUE minterms

<i>A</i>	<i>R</i>	<i>E</i>
0	0	1
0	1	0
1	0	0
1	1	0

Figure 2.10 Ben's truth table

 

(a)

 

(b)

Figure 2.11 Ben's circuit

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


Figure 2.12 Random three-input truth table

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

Figure 2.13 Truth table with multiple FALSE maxterms




(a)

 


(b)

Figure 2.14 Identity theorem in hardware: (a) $T1$, (b) $T1'$

 

(a)

 

(b)

Figure 2.15 Null element theorem in hardware: (a) T2, (b) T2'



(a)



(b)

Figure 2.16 Idempotency theorem in hardware: (a) T3, (b) T3'



 


Figure 2.17 Involution theorem in hardware: T4

 



(a)

 

(b)

Figure 2.18 Complement theorem in hardware: (a) T5, (b) T5'



NAND

  

$$Y = \overline{AB} = \overline{A} + \overline{B}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR

  

$$Y = \overline{A + B} = \overline{A} \overline{B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Figure 2.19 De Morgan equivalent gates

A	B	Y	\bar{Y}
0	0	0	1
0	1	0	1
1	0	1	0
1	1	1	0

Figure 2.20 Truth table showing Y and \bar{Y}

A	B	Y	\bar{Y}	minterm
0	0	0	1	$\bar{A} \bar{B}$
0	1	0	1	$\bar{A} B$
1	0	1	0	$A \bar{B}$
1	1	1	0	$A B$

Figure 2.21 Truth table showing minterms for \bar{Y}

B	C	D	$BC + \bar{B}D + CD$	$BC + \bar{B}D$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	1
1	0	0	0	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	1

Figure 2.22 Truth table proving T11


 


Figure 2.23 Schematic of $Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C}$

wires connect
at a T junction

 

wires connect
at a dot



wires crossing
without a dot do
not connect



Figure 2.24 Wire connections

 


Figure 2.25 Schematic of $Y = \overline{B} \overline{C} + A \overline{B}$


 


Figure 2.26 Schematic using fewer gates

 

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

Figure 2.27 Priority circuit

 


Figure 2.28 Priority circuit schematic

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

Figure 2.29 Priority circuit truth table with don't cares (X's)

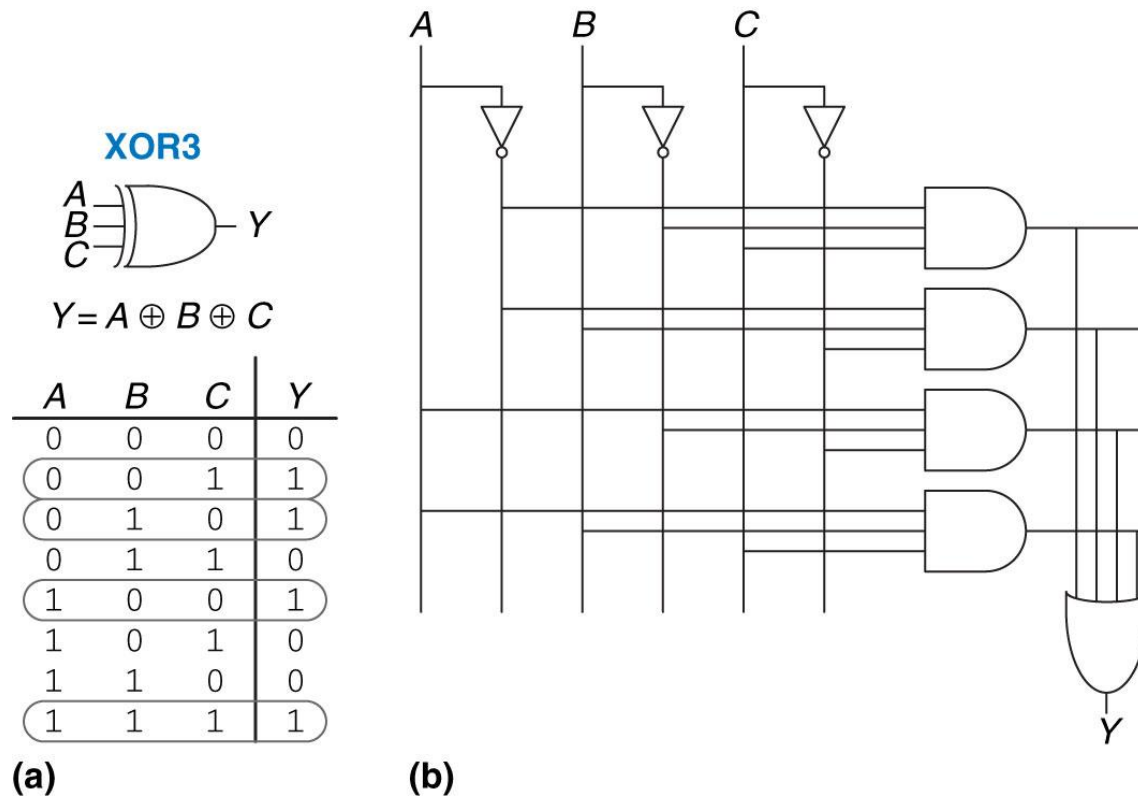


Figure 2.30 Three-input XOR: (a) functional specification and (b) two-level logic implementation

 


Figure 2.31 Three-input XOR using two-input XORs

 


Figure 2.32 Eight-input XOR using seven two-input XORs

 


Figure 2.33 Multilevel circuit using NANDs and NORs

 
 
 


Figure 2.34 Bubble-pushed circuit

 


Figure 2.35 Logically equivalent bubble-pushed circuit

 


Figure 2.36 Circuit using ANDs and ORs



 


Figure 2.37 Poor circuit using NANDs and NORs

 

(a)

 

(b)

Figure 2.38 Better circuit using NANDs and NORs


 



Figure 2.39 Circuit with contention

Tristate Buffer

 

E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

Figure 2.40 Tristate buffer

 

\bar{E}	A	Y
0	0	0
0	1	1
1	0	Z
1	1	Z

Figure 2.41 Tristate buffer with active low enable

 


Figure 2.42 Tristate bus connecting multiple chips

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

(a)

Y		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

(b)

Y		AB			
		00	01	11	10
C	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

(c)

Figure 2.43 Three-input function: (a) truth table, (b) K-map, (c) K-map showing minterms

 


Figure 2.44 K-map minimization

		Y			
		AB			
		00	01	11	10
C	0	1	0	1	1
	1	1	0	0	1

Figure 2.45 K-map for Example 2.9

 


Figure 2.46 Solution for Example 2.9

 


Figure 2.47 Seven-segment display decoder icon

 


Figure 2.48 Seven-segment display digits

S_a		$D_{3:2}$			
		$D_{1:0}$	00	01	11
$D_{1:0}$	00	1	0	0	1
	01	0	1	0	1
	11	1	1	0	0
	10	1	1	0	0

S_b		$D_{3:2}$			
		$D_{1:0}$	00	01	11
$D_{1:0}$	00	1	1	0	1
	01	1	0	0	1
	11	1	1	0	0
	10	1	0	0	0

Figure 2.49 Karnaugh maps for S_a and S_b

 


Figure 2.50 K-map solution for Example 2.10

 


Figure 2.51 Alternative K-map for S_a showing different set of prime implicants



 


Figure 2.52 Alternative K-map for S_a showing incorrect nonprime implicant

 

 
$$S_a = D_3 + D_2 D_0 + \bar{D}_2 \bar{D}_0 + D_1$$



$$S_b = \bar{D}_2 + D_1 D_0 + \bar{D}_1 \bar{D}_0$$

Figure 2.53 K-map solution with don't cares

 

S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Figure 2.54 2:1 multiplexer symbol and truth table


 
 


Figure 2.55 2:1 multiplexer implementation using two-level logic

 

$$Y = D_0 \bar{S} + D_1 S$$

Figure 2.56 Multiplexer using tristate buffers

 


Figure 2.57 4:1 multiplexer

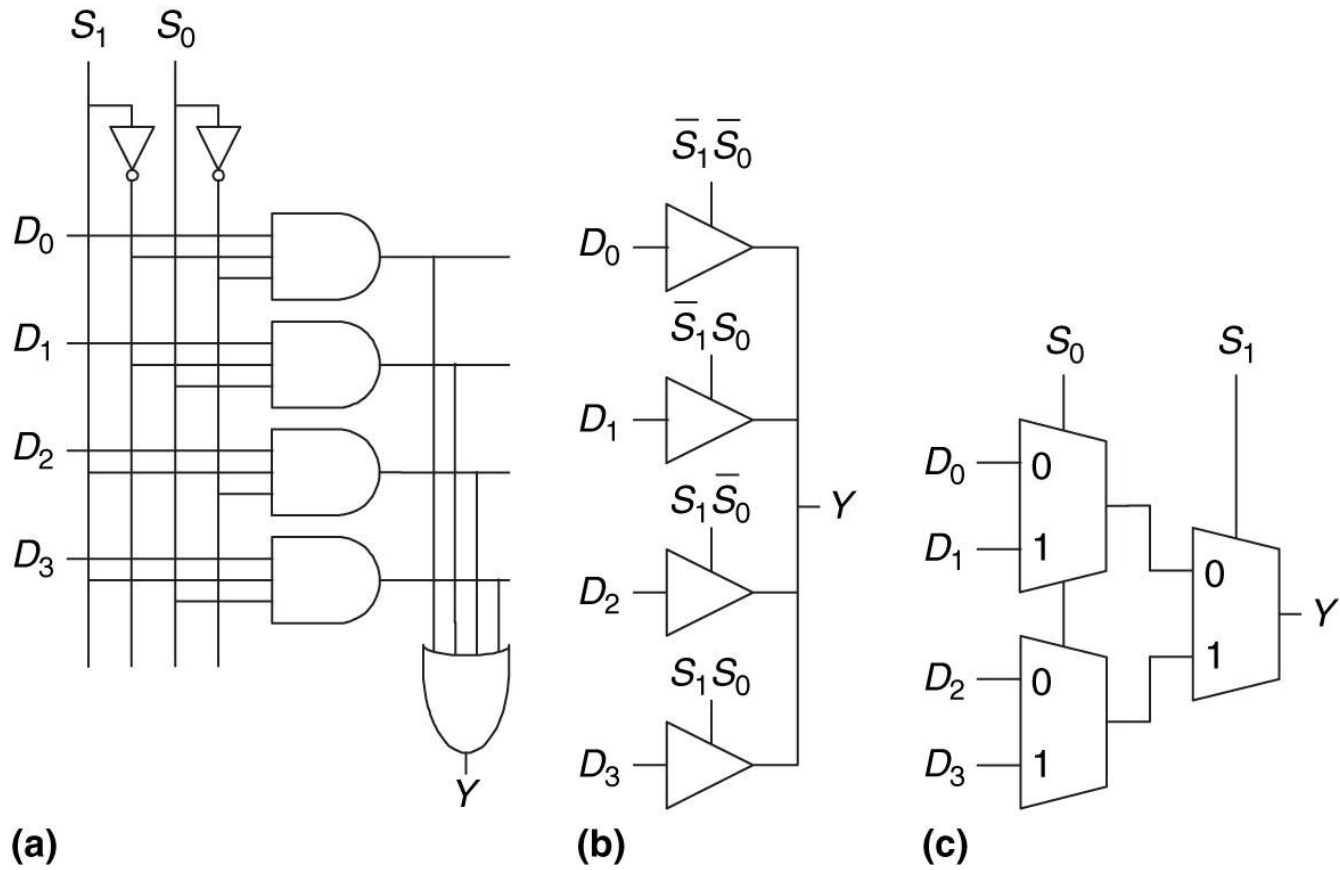


Figure 2.58 4:1 multiplexer implementations: (a) two-level logic, (b) tristates, (c) hierarchical

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

$Y = AB$

 


Figure 2.59 4:1 multiplexer implementation of two-input AND function


 


Figure 2.60 Multiplexer logic using variable inputs

<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$

(a)

 

(b)

Figure 2.61 Alyssa's circuit: (a) truth table, (b) 8:1 multiplexer implementation

 
 


Figure 2.62 Alyssa's new circuit

 


Figure 2.63 2:4 decoder

 


Figure 2.64 2:4 decoder implementation

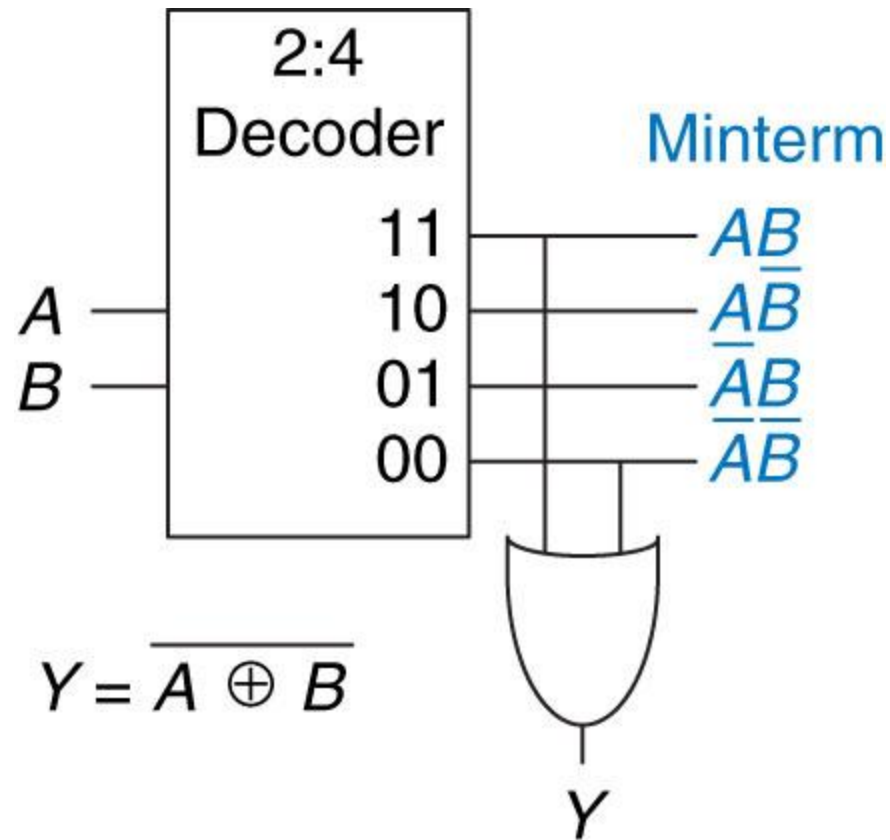


Figure 2.65 Logic function using decoder

 


Figure 2.66 Circuit delay

 


Figure 2.67 Propagation and contamination delay

 


Figure 2.68 Short path and critical path

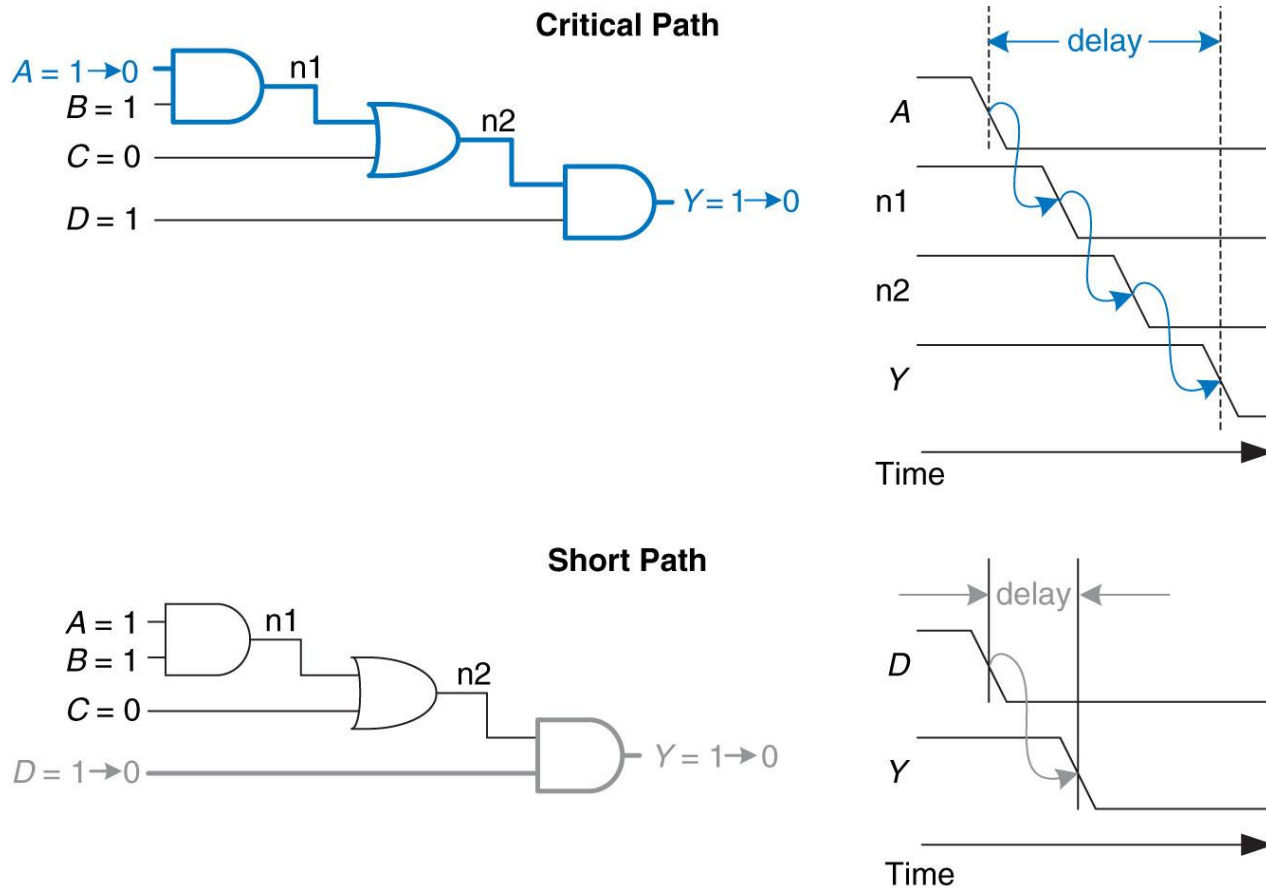


Figure 2.69 Critical and short path waveforms

 


Figure 2.70 Ben's circuit

 


Figure 2.71 Ben's critical path

 


Figure 2.72 Ben's shortest path


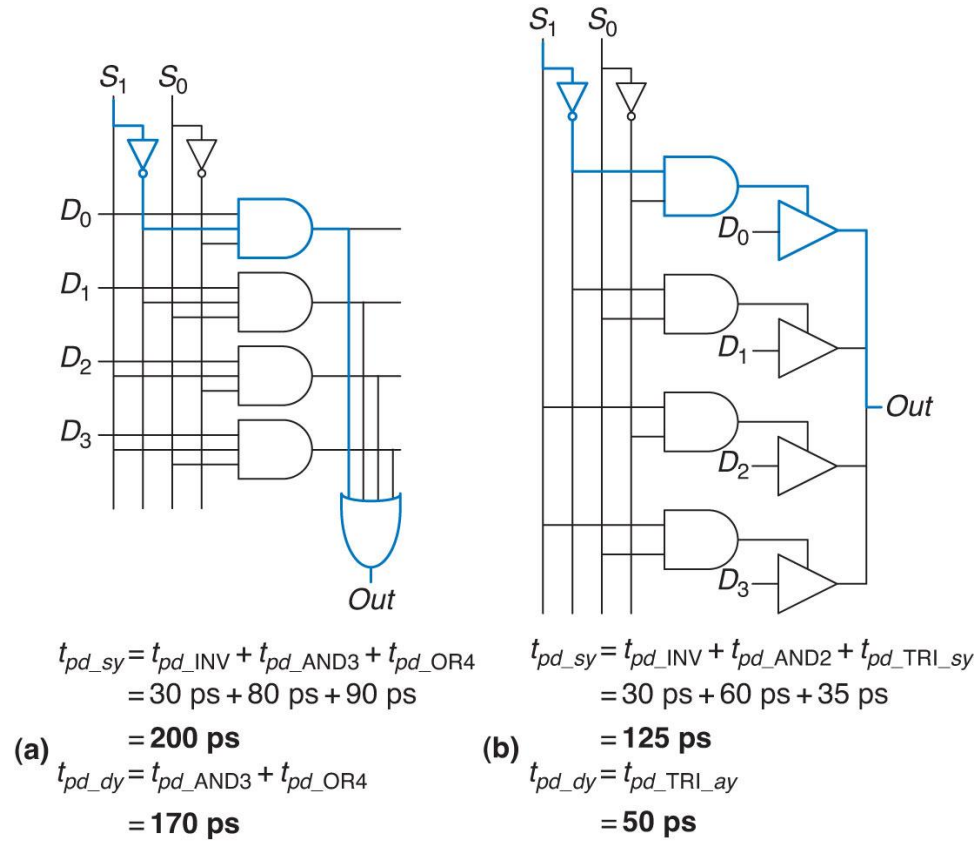



Figure 2.73 4:1 multiplexer propagation delays: (a) two-level logic, (b) tristate

 

$$t_{pd_s0y} = t_{pd_TRLSY} + t_{pd_TRI_AY} = \mathbf{85\ ns}$$

$$t_{pd_dy} = 2\ t_{pd_TRI_AY} = \mathbf{100\ ns}$$

Figure 2.74 4:1 multiplexer propagation delays: hierarchical using 2:1 multiplexers

 

Y

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$

Figure 2.75 Circuit with a glitch

 


Figure 2.76 Timing of a glitch

 


Figure 2.77 Input change crosses implicant boundary

 


Figure 2.78 K-map without glitch

 


Figure 2.79 Circuit without glitch

(a)			(b)				(c)				(d)					(e)				
A	B	Y	A	B	C	Y	A	B	C	Y	A	B	C	D	Y	A	B	C	D	Y
0	0	1	0	0	0	1	0	0	0	1	0	0	0	0	1	0	0	0	0	1
0	1	0	0	0	1	0	0	0	1	0	0	0	0	1	1	0	0	0	1	0
1	0	1	0	1	0	0	0	1	0	1	0	0	1	0	1	0	0	1	0	0
1	1	1	0	1	1	0	0	1	1	0	0	0	1	1	1	0	0	1	1	1
			1	0	0	0	1	0	0	1	0	1	0	0	0	0	1	0	0	0
			1	0	1	0	1	0	1	1	0	1	0	1	0	0	1	0	1	1
			1	1	0	0	1	1	0	0	0	1	1	0	0	0	1	1	0	1
			1	1	1	1	1	1	1	1	0	1	1	1	0	0	1	1	1	0
											1	0	0	0	1	1	0	0	0	0
											1	0	0	1	0	1	0	0	1	1
											1	0	1	0	1	1	0	1	0	1
											1	1	0	0	0	1	1	0	0	1
											1	1	0	1	0	1	1	0	1	0
											1	1	1	0	1	1	1	0	0	0
											1	1	1	1	0	1	1	1	1	1

Figure 2.80 Truth tables for Exercises 2.1 and 2.3

(a)			(b)				(c)				(d)					(e)				
<i>A</i>	<i>B</i>	<i>Y</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	1	1	0	0	1	1	0	0	0	1	0	0	0	0	1	0
1	0	1	0	1	0	1	0	1	0	0	0	0	1	0	1	0	0	1	0	0
1	1	1	0	1	1	1	0	1	1	0	0	0	1	1	1	0	0	1	1	1
			1	0	0	1	1	0	0	0	0	1	0	0	0	0	1	0	0	0
			1	0	1	0	1	0	1	0	0	0	1	0	1	0	1	0	1	0
			1	1	0	1	1	1	0	1	0	1	1	0	1	0	1	1	1	1
			1	1	1	0	1	1	1	1	0	1	1	1	1	0	1	1	1	1
											1	0	0	0	1	1	0	0	0	1
											1	0	0	1	0	1	0	0	1	1
											1	0	1	0	1	1	0	1	1	1
											1	0	1	1	0	1	1	0	0	0
											1	1	0	1	0	1	1	0	1	0
											1	1	1	0	0	1	1	1	0	0
											1	1	1	1	0	1	1	1	1	0

Figure 2.81 Truth tables for Exercises 2.2 and 2.4

 


Figure 2.82 Circuit schematic

 


Figure 2.83 Circuit schematic

 


Figure 2.84 Circuit schematic

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	X
0	0	0	1	X
0	0	1	0	X
0	0	1	1	0
0	1	0	0	0
0	1	0	1	X
0	1	1	0	0
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

Figure 2.85 Truth table for Exercise 2.28

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	X
0	0	1	1	X
0	1	0	0	0
0	1	0	1	X
0	1	1	0	X
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

Figure 2.86 Truth table for Exercise 2.31

 


Figure 2.87 Multiplexer circuit

 


Figure 2.88 Multiplexer circuit


 


Figure M 01

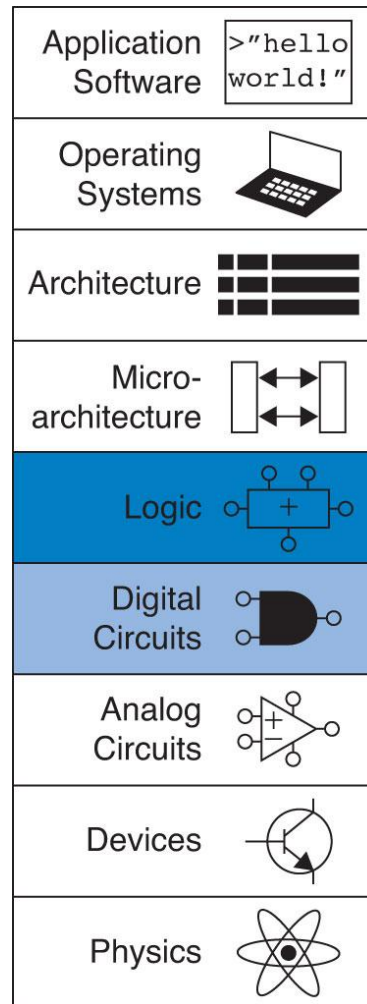

Figure M 02



UNN Figure 1